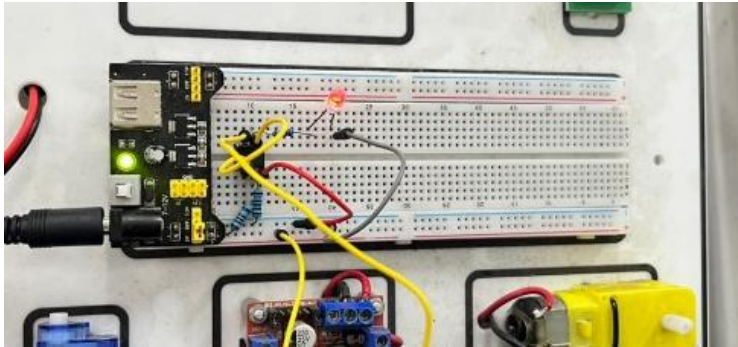


LAPORAN PROYEK 1A



Nama : Siti Mutiara Putri (27125055), Delvia Nandarizka Anida (27125041)

Kelas : 4KB06

1. Rangkaian LED (ON)



2. Rangkaian Simulator Falstad

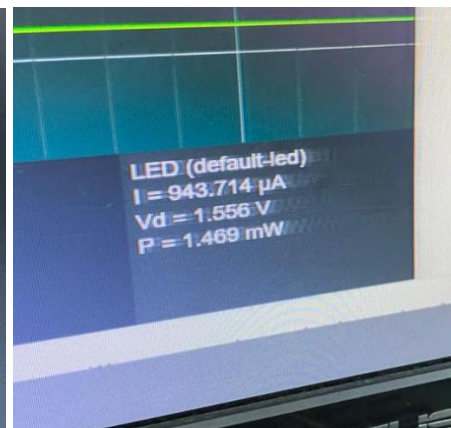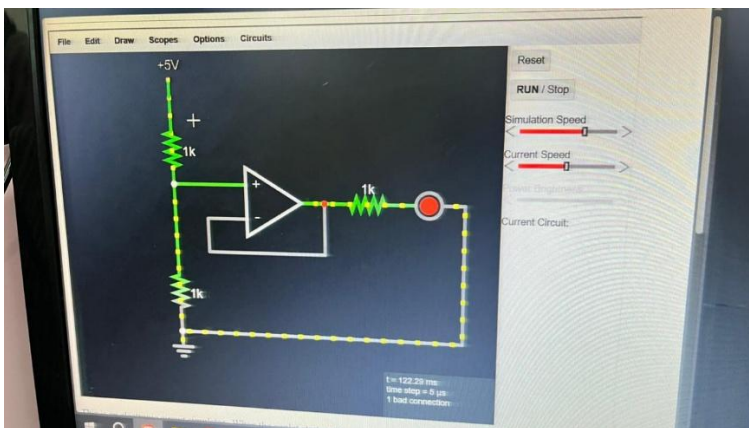

3. Nilai-nilai dengan Multimeter

R1



R2



R3



Arus



Arus Output



Perhitungan

No
Date

Nama :- Delvia Nandazka Anida
- Siti Mutiara Putri

1). Rumus : $V_{in} = V_s \times \frac{R_1}{R_1 + R_2}$ (pembagi tegangan)

Diket : $V_s = 5V$
 $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$


Dit : $V_{in} = 5 \times \frac{1000}{1000 + 1000}$
 $= 5 \times \frac{1000}{2000}$
 $= 5 \times 0,5$
 $= 2,5 \text{ V}$
//

2). Rumus $V_{out} : V_{out} = V_{in} \Rightarrow V_{out} = 2,5 \text{ V}$

LAPORAN PROYEK 1B

1. Dokumentasi Percobaan Gelombang OSCL

No 7 (Delvia Nandarizka Anida)

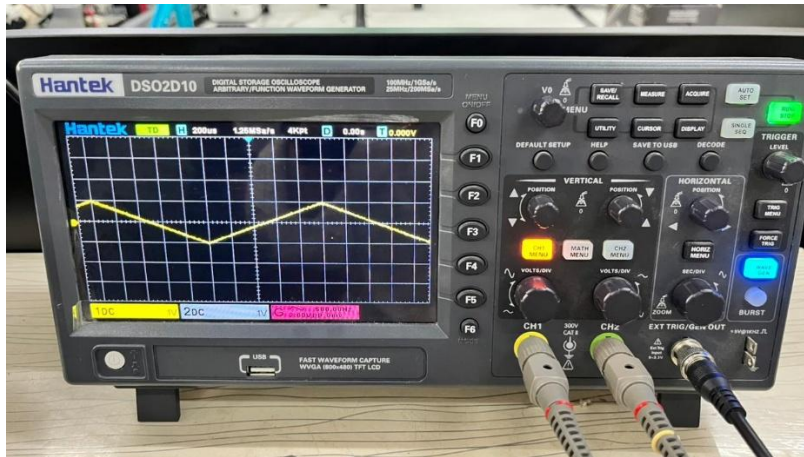

No 8 (Siti Mutiara Putri)

